

Series and Parallel Circuits

1. State two characteristics of (i) a series circuit and (ii) a parallel circuit.

2. What happens to the total current that flows in a
 - (a) series circuit if another load is connected in series with the existing loads?

 - (b) parallel circuit if another load is connected in parallel with the existing loads?

3. What effect does the change in current have on the effective resistance of the total circuit in 2 (a) and (b)?

4. Draw a schematic circuit diagram for each of the following:
 - (a) Three dry cells are connected in series, which in turn are connected to two light bulbs, a motor, and a switch, also connected in series. A voltmeter is connected to the battery to measure its voltage.

 - (b) Two dry cells are connected in series, which in turn are connected to three light bulbs in parallel. A switch can control just one of the light bulbs. An ammeter measures the current of the entire circuit.

